

Simulate using Tinkercad to measure the voltage (V_a). Show the screenshot of Tinkercad.

